

Chapter 30

Inductance and Electromagnetic Oscillations

Units of Chapter 30

- 30.1 Mutual Inductance: 1
- 30.2 Self-Inductance: 2, 3, & 4
- 30.3 Energy Stored in a Magnetic Field: 5, 6, & 7
- 30.4 LR Circuit: 8, 9, & 10
- 30.5 LC Circuits and Electromagnetic Oscillations: 11, 12, & 13
- 30.6 LC Oscillations with Resistance (LRC Circuit): 14 & 15

- Faraday's Law: Changing current in a circuit will induce emf in that circuit as well as others nearby
- Self-Inductance: Circuit induces emf in itself
- Mutual Inductance: Circuit induces emf in second circuit

30-1 Mutual Inductance

emf induced in circuit 2 by changing currents in circuit 1, through mutual inductance:

$$\mathcal{E}_{21} = -M \frac{dI_1}{dt}$$

- The mutual inductance M depends only on the geometry of the two-circuit system
- subscripts are omitted, as $M_{21} = M_{12}$

Pre Inductance Review

Review the BIG 4 (Gauss², Faraday, Amperes)

Determine B for a solenoid

Solve for the current in the solenoid


Determine the magnetic flux in the solenoid

Determine the self inductance

$$1 \text{ H} = 1 \text{ Wb/A} = 1 \text{ T} \cdot \text{m}^2/\text{A} = 1 \Omega \cdot \text{s}$$

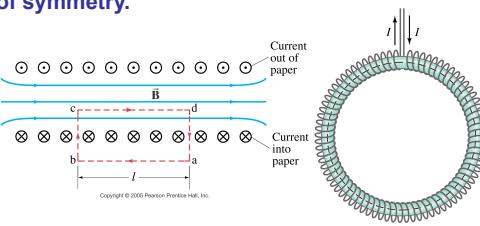28.5 Magnetic Field of a Solenoid and a Toroid

Ampère's law can be used to calculate the magnetic field in situations with a high degree of symmetry.



Solenoids

$$\oint B \cdot d\ell = \int_a^b B \cdot d\ell + \int_b^c B \cdot \vec{d\ell} + \int_c^d B \cdot d\ell + \int_d^a B \cdot \vec{d\ell}$$

$B \rightarrow 0$ $\cos 90^\circ = 0$ $\cos 90^\circ = 0$

$$\oint B \cdot d\ell = \int_c^d B \cdot d\ell = Bl = \mu_0 I_{\text{enc}}$$

$$Bl = \mu_0 N I \Rightarrow B = \frac{\mu_0 N I}{l} = \mu_0 n I$$

IMPORTANT NOTE: n is equal to the number of loops per unit length (aka. Loop Density). It is NOT the number of wires!

30-1 Mutual Inductance

Units of inductance: Henry

$$1 \text{ H} = 1 \text{ Wb/A} = 1 \text{ T} \cdot \text{m}^2/\text{A} = 1 \Omega \cdot \text{s}$$

Mutual Inductance

defined as

$$M_{21} = \frac{N_2 \Phi_{21}}{I_1}$$

$$\mathcal{E}_2 = -N_2 \frac{d\Phi_{21}}{dt}$$

$$\Rightarrow \Phi_{21} = \frac{M_{21} I_1}{N_2} \Rightarrow \frac{d\Phi_{21}}{dt} = \frac{M_{21}}{N_2} \frac{dI_1}{dt}$$

$$\mathcal{E}_2 = -M_{21} \frac{dI_1}{dt}$$

Transformers

30-2 Self-Inductance

emf induced through self-inductance:

$$\mathcal{E} = -\frac{d\Phi_B}{dt} = -L \frac{dI}{dt}$$

The inductance L is a proportionality constant that depends on the geometry of the circuit

Magnetic materials will change self-inductance by changing magnetic flux

Mutual Inductance vs. Self-Inductance

Chapter 30

$$M = \frac{N_2 \Phi_{2i}}{I_1}$$

$$\mathcal{E}_2 = -N_2 \frac{d\Phi_{2i}}{dt} = -M \frac{dI_1}{dt}$$

$$L = \frac{N \Phi_B}{I}$$

$$\mathcal{E} = -N \frac{d\Phi_B}{dt} = -L \frac{dI}{dt}$$

30-3 Energy Stored in a Magnetic Field

- Work must be done to create current through inductor
- This changes the energy stored in the inductor
- Starting from zero current:

$$U_L = \frac{1}{2} L I^2$$

30-3 Energy Stored in a Magnetic Field

The energy in a solenoid depends on the current, and therefore on the magnetic field created by the current:

$$U_L = \frac{1}{2} \frac{B^2}{\mu_0} A\ell$$


giving the energy density of the magnetic field:

$$u_B = \frac{1}{2} \frac{B^2}{\mu_0}$$

Inductance Practice (Homework)

- Ex. 30-1 Solenoid and coil (§ 30-1)
- Ex. 30-2 Direction of emf in a solenoid (§ 30-2)
- Ex. 30-3 Solenoid inductance (§ 30-2)
- Energy stored in a solenoid (§ 30-3)
- Energy density in a solenoid's magnetic field (§ 30-3)
- Ex. 30-4 Coaxial cable inductance (§ 30-2)
- Ex. 30-5 Energy stored in a coaxial cable (§ 30-3)


30-4 LR Circuits

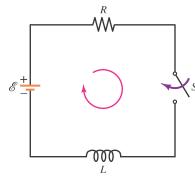

Copyright © 2008 Pearson Prentice Hall, Inc.

When the switch closes, the inductor keeps the current from attaining its maximum value immediately. That is when the current is changing most rapidly, and when the potential drop across the conductor is at a maximum.

30-4 LR Circuits

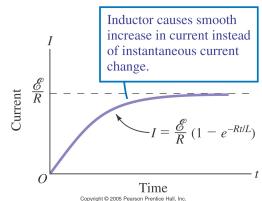


Current as a function of time:

$$I = \frac{E}{R} [1 - e^{-t/(L/R)}] = \frac{E}{R} (1 - e^{-Rt/L})$$

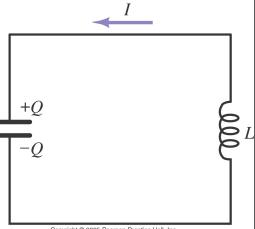30-5 Oscillations in LC Circuits and Electromagnetic Oscillations

- Start with charged capacitor
- It will discharge through inductor, and then recharge in opposite sense
- If no resistance, will continue indefinitely



30-5 Oscillations in LC Circuits and Electromagnetic Oscillations

Charge on capacitor oscillates with frequency ω :


$$\omega = \frac{1}{\sqrt{LC}}$$

Charge as a function of time:

$$Q = Q_0 \cos(\omega t + \phi)$$

Here, Q_0 is the original charge and ϕ sets the phase at $t = 0$.

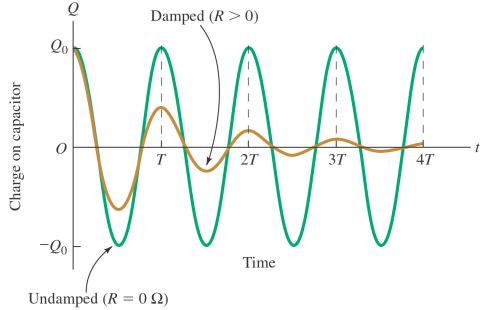30-6 LC Oscillations with Resistance (LCR Circuits)



30-6 LC Oscillations with Resistance (LCR Circuits)

Charge equation: $L \frac{d^2Q}{dt^2} + R \frac{dQ}{dt} + \frac{Q}{C} = 0$

Solution: $Q = Q_0 e^{-\alpha t} \cos(\omega' t + \phi)$


where $\alpha = \frac{R}{2L}$

and $\omega'^2 = \frac{1}{LC} - \frac{R^2}{4L^2} = \frac{1}{LC} - \alpha^2 = \omega^2 - \alpha^2$

30-6 LC Oscillations with Resistance (LCR Circuits)

For a certain value of R , $\omega' = 0$. This is called critical damping.

$$R_c = 2 \sqrt{\frac{L}{C}}$$

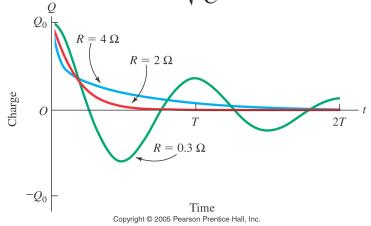

30-6 LC Oscillations with Resistance (*LRC* Circuits)

- In a pure *LC* circuit, energy is transferred back and forth between the capacitor's electric field and the inductor's magnetic field.
- Including a resistor causes I^2R losses, which show up as heat.

Homework: Inductance Practice

- Ex. 30-1 Solenoid and coil (§ 30-1)
- Ex. 30-2 Direction of emf in a solenoid (§ 30-2)
- Ex. 30-3 Solenoid inductance (§ 30-2)
- Energy stored in a solenoid (§ 30-3)
- Energy density in a solenoid's magnetic field (§ 30-3)
- Ex. 30-4 Coaxial cable inductance (§ 30-2)
- Ex. 30-5 Energy stored in a coaxial cable (§ 30-3)

Homework: Derivations for Inductance

- *LR* Circuit (§ 30-4)
- *LC* Circuit (§ 30-5)
- *LRC* Circuit (§ 30-6)

Summary of Chapter 30

- **Definition of inductance:** $\Phi_B = LI$
- **Induced emf:** $\mathcal{E} = -\frac{d\Phi_B}{dt} = -L \frac{dI}{dt}$
- **emf induced in a second loop:** $\mathcal{E}_{21} = -M \frac{dI_1}{dt}$
- **Energy in an inductor:** $U_L = \frac{1}{2}LI^2$
- **Energy density of a magnetic field:** $u_B = \frac{1}{2} \frac{B^2}{\mu_0}$

Summary of Chapter 30, cont.

• **LC circuit oscillations:** $\omega = \frac{1}{\sqrt{LC}}$

• **LRC circuit oscillations:**

$$Q = Q_0 e^{-\alpha t} \cos(\omega' t + \phi)$$

30.1

$$\mathcal{E}_2 = -M_{21} \frac{dI_1}{dt} \quad \mathcal{E}_1 = -M_{12} \frac{dI_2}{dt}$$

$$M_{21} = M_{12} = M$$


$$\mathcal{E}_2 = -M \frac{dI_1}{dt} \quad \mathcal{E}_1 = -M \frac{dI_2}{dt}$$

$$1 \text{ H} = 1 \frac{\text{V}\cdot\text{s}}{\text{A}} = 1 \Omega \cdot \text{s} \quad (\text{Unit for inductance})$$

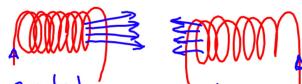30.2

Self Inductance, L

$$L = N \frac{\Phi_B}{I} ; \quad \Sigma = -N \frac{d\Phi_B}{dt} = L \frac{dI}{dt}$$



Created / Induced
solenoids in circuits are inductors

30.3 Energy Stored in the B-Field

$$P = IV = Ie = IL \frac{dI}{dt}$$

$$E = -L \frac{dI}{dt}$$

$$\frac{dW}{dt} = P \Rightarrow \int_0^{\omega} dW = P dt = \int_0^I IL \frac{dI}{dt} dt = \int_0^I I dI$$

$$W = \frac{1}{2} L (I^2) \quad L = M_o \frac{N^2 A}{\ell} \quad B = \mu_o N I$$

$$W = \frac{1}{2} \left(M_o \frac{N^2 A}{\ell} \right) \left(\frac{B^2 \ell^2}{\mu_o N^2} \right) = \frac{1}{2} \frac{B^2 \ell}{M_o} AL$$

$$I = \frac{B \ell}{\mu_o N}$$

3D.3 Energy Stored in the B-Field

$$P = IV = I\mathcal{E} = IL \frac{dI}{dt} \quad \text{where } \mathcal{E} = L \frac{dI}{dt}$$

Need to Know:

$$\frac{d\omega}{dt} = P ; \quad L_{Solenoid} = \mu_0 \frac{N^2 A}{l} ; \quad B = \mu_0 \frac{NI}{l} \Rightarrow I = \frac{Bl}{\mu_0 N}$$

$$\int_{\text{d}t}^{\text{d}W} = P \text{d}t = \int_{\text{d}I}^I L \frac{\text{d}I}{\text{d}t} dt = L \int_{\text{d}I}^I I \text{d}I = \frac{1}{2} L I^2$$

$$U = \frac{1}{2} L I^2 = \frac{1}{2} \left(\frac{M_0 N^2 A}{\lambda} \right) \left(\frac{B^2 \lambda^2}{M_0 N^2} \right) = \frac{1}{2} \frac{B^2}{M_0} A I$$

U = energy density = $\frac{U}{Volume} = \frac{1}{2} \frac{B^2}{M_0}$ Similar to $u \propto \frac{1}{2} E^2$

$$u = \text{energy density} = \frac{U}{\text{Volume}} = \frac{1}{2} \frac{B^2}{M_0} \quad \text{similar to } u = \frac{1}{2} \epsilon_0 E^2$$

Important Derivatives:


$$\frac{d}{dt} [Q^2] = 2Q \frac{dQ}{dt}$$

$$\frac{d}{dt} [I^2] = 2I \frac{dI}{dt}$$

$$I^2$$

$$\frac{dI}{dt} = 2I$$

304 LR Circuit

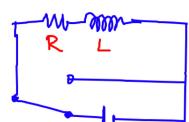

Kirchhoff's Loop Rule


$$E - IR - L \frac{dI}{dt} = 0$$

$$E - IR = L \frac{dI}{dt}$$

$$(E - IR) dt + L dI \Rightarrow \frac{1}{L} \int dt = \int \frac{1}{E - IR} dI$$

$$\frac{1}{L} t = -\frac{1}{R} \ln(E - IR)$$

304 LR Circuit

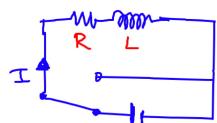

$$\frac{1}{L} t = -\frac{1}{R} \ln \left(\frac{E - IR}{E} \right)$$




Solve for I




$$-\frac{R}{L} t = \ln \left(\frac{E - IR}{E} \right)$$

$$\frac{E - IR}{E} = e^{-\frac{R}{L} t} \Rightarrow E - IR = E e^{-\frac{R}{L} t}$$


$$E - E e^{-\frac{R}{L} t} = IR \Rightarrow I = \frac{E}{R} (1 - e^{-\frac{R}{L} t})$$

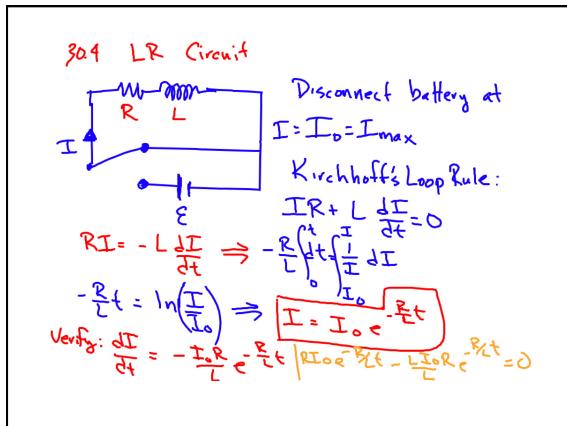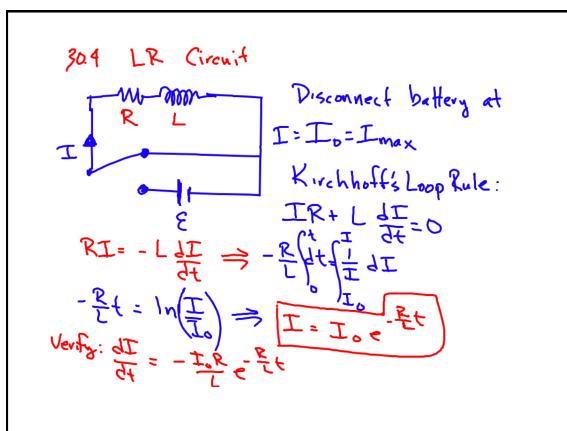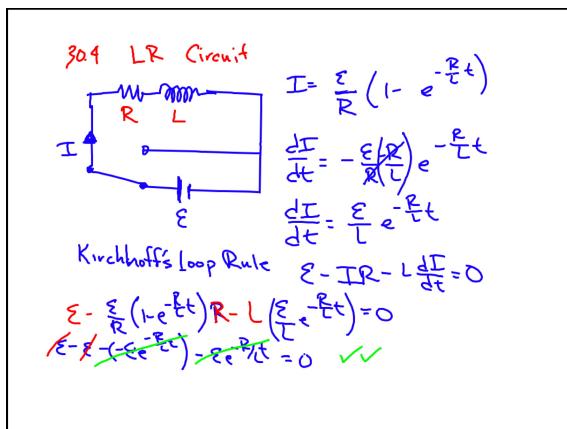$\gamma = \frac{R}{L}$ time constant for LR circuit



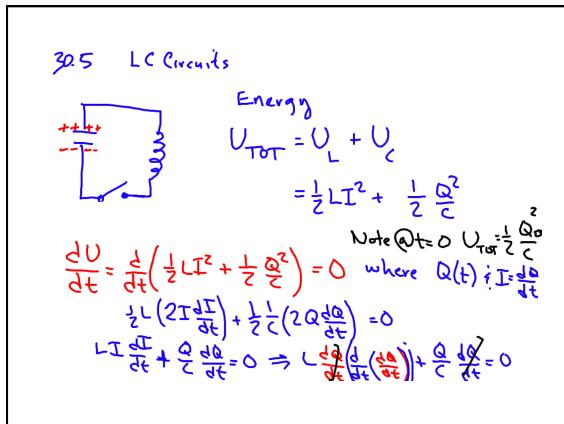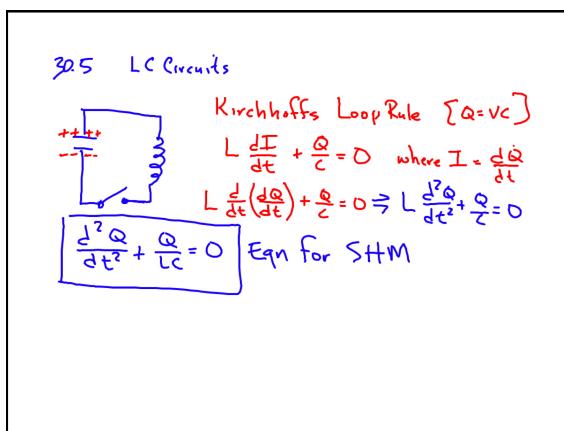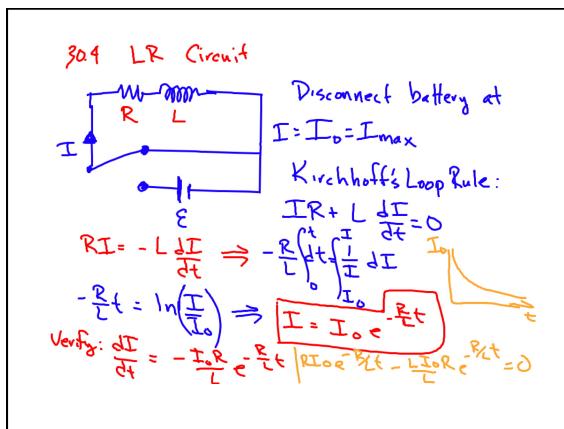

30.5 LC Circuits

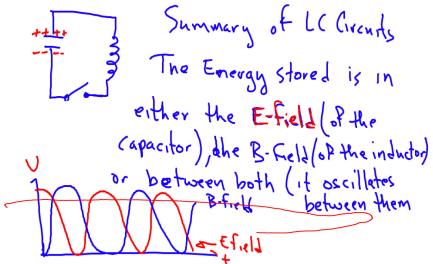

30.6 LRC Circuits

Kirchhoff's Loop Rule

$$-L \frac{dI}{dt} - IR + \frac{1}{C} Q = 0$$

$$-L \frac{d}{dt} \left(-\frac{dQ}{dt} \right) - \left(\frac{1}{C} \right) R + \frac{1}{C} Q = 0$$

$$L \frac{d^2Q}{dt^2} + R \frac{dQ}{dt} + \frac{1}{C} Q = 0 \quad \text{Eqn for a damped harmonic oscillator (DHO)}$$

Soln for DHO: $Q = Q_0 e^{-\alpha t} \cos(\omega t)$

Conservation of Energy

$$\frac{dU}{dt} = \frac{d}{dt} \left(\frac{1}{2} LI^2 + \frac{1}{2} \frac{Q^2}{C} \right) = -I^2 R$$

$$\frac{1}{2} L 2I \frac{dI}{dt} + \frac{1}{2} C 2Q \frac{dQ}{dt} = -I^2 R$$

$$LI \frac{dI}{dt} + \frac{Q}{C} \frac{dQ}{dt} = -I^2 R \quad \text{where } I = \frac{dQ}{dt}$$

$$L \frac{dI}{dt} \frac{d \left(\frac{dQ}{dt} \right)}{dt} + \frac{Q}{C} \frac{dQ}{dt} = - \frac{dQ}{dt} \frac{dQ}{dt} R$$

$$L \frac{d^2Q}{dt^2} + R \frac{dQ}{dt} + \frac{1}{C} Q = 0$$

$$Q = Q_0 e^{-\alpha t} \cos(\omega' t)$$

$$\frac{dQ}{dt} = -\alpha Q_0 e^{-\alpha t} \cos(\omega' t) - \omega' Q_0 e^{-\alpha t} \sin(\omega' t)$$

$$\frac{d^2 Q}{dt^2} = \alpha^2 Q_0 e^{-\alpha t} \cos(\omega' t) + \alpha \omega' Q_0 e^{-\alpha t} \sin(\omega' t) \\ + \alpha \omega' Q_0 e^{-\alpha t} \sin(\omega' t) - \omega'^2 Q_0 e^{-\alpha t} \cos(\omega' t)$$

$$\frac{d^2 Q}{dt^2} = 2\alpha \omega' Q_0 e^{-\alpha t} \sin(\omega' t) + (\alpha^2 - \omega'^2) Q_0 e^{-\alpha t} \cos(\omega' t)$$

Substitute above back into

$$L \frac{d^2 Q}{dt^2} + R \frac{dQ}{dt} + \frac{1}{C} Q = 0$$

$$L (2\alpha \omega' Q_0 e^{-\alpha t} \sin(\omega' t) + (\alpha^2 - \omega'^2) Q_0 e^{-\alpha t} \cos(\omega' t)) \\ + R (-\omega' Q_0 e^{-\alpha t} \sin(\omega' t) - \alpha Q_0 e^{-\alpha t} \cos(\omega' t)) \\ + \frac{1}{C} (Q_0 e^{-\alpha t} \cos(\omega' t)) = 0$$

$$(2L\alpha\omega - R\omega') Q_0 e^{-\alpha t} \sin(\omega' t) \\ + (L\alpha^2 - L\omega'^2 - R\alpha + \frac{1}{C}) Q_0 e^{-\alpha t} \cos(\omega' t) = 0$$

$$(2L\alpha\omega - R\omega') Q_0 e^{-\alpha t} \sin(\omega' t) \quad \text{at } t=0$$

$$(L\alpha^2 - L\omega'^2 - R\alpha + \frac{1}{C}) Q_0 e^{-\alpha t} \cos(\omega' t) = 0$$

at $t = \frac{\pi}{2} \omega'$; $\cos(\omega' t) = 0$ Solve for α

$$2L\alpha\omega - R\omega' = 0 \Rightarrow \boxed{\alpha = \frac{R}{2L}} \quad \gamma = \frac{2L}{R}$$

at $t = 0$; $\sin(\omega' t) = 0$ Solve for ω'

$$L\alpha^2 - L\omega'^2 - R\alpha + \frac{1}{C} = 0$$

$$\omega'^2 = \alpha^2 - \frac{R}{L}\alpha + \frac{1}{LC} = \frac{R^2}{4L^2} - \frac{R^2}{2L^2} + \frac{1}{LC} = \frac{1}{LC} - \frac{R^2}{4L^2}$$

$$\omega' = \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}}$$

$$\omega = \sqrt{\frac{1}{LC} - \frac{R^2}{4L^2}} \Rightarrow \frac{1}{LC} - \frac{R^2}{4L^2} = 0 \Rightarrow R^2 = \frac{4L}{C}$$

If $R = \sqrt{\frac{4L}{C}}$ critically damped doesn't oscillate

$R < \sqrt{\frac{4L}{C}}$ under damped oscillates for a long time

$R > \sqrt{\frac{4L}{C}}$ over damped  doesn't return to center for a long time

Modification of Kirchhoff's loop rule:

In moving across an inductor of inductance L along (or against) the presumed direction of the current I , the potential change is $\Delta V = -L \frac{dI}{dt}$ (or $+L \frac{dI}{dt}$, respectively). -el fin aside-

Kirchhoff's Loop Rule

$$-L \frac{dI}{dt} - IR + \frac{1}{C} Q = 0 \quad \text{where } I = -\frac{dQ}{dt}$$

$$-L \left(-\frac{d^2 Q}{dt^2} \right) - \left(\frac{dQ}{dt} \right) R + \frac{1}{C} Q = 0$$

$$\boxed{L \frac{d^2 Q}{dt^2} + R \frac{dQ}{dt} + \frac{1}{C} Q = 0}$$